

# CDA 4213/CIS 6930 CMOS VLSI

## Fall 2024

### Final Project

#### Due date(s)

Friday, 6<sup>th</sup> December 2024

Today's Date:	December 5 <sup>th</sup> , 2024
Your Team Name:	<i>The Floral Princesses</i>
Team Members:	<i>Aidan Khalil – U9240-8495</i> <i>Sergio Flores – U9506-2088</i>
Work Distribution	<b><i>Explain in detail who has done what. Each team member's grade will be based on their overall contribution.</i></b>  <i>1) Aidan Khalil – nand, inverter, full adder, 4x4 multiplier</i>  <i>2) Sergio Flores – and, mux, input / output registers, testing</i>
No. of Hours Spent:	50
Exercise Difficulty: (Easy, Average, Hard)	Average
Any Feedback:	N/A

**(10 pts) Proposed Design – Bit slice design**

(a) List all module bit-slices you have used for your design. ✓

**- x1 4x4 multiplier (16 ANDs + 20 Full Adders)**

**- x9 MUXs (for selections)**


**- x2 sets of 4-bit shift registers (SIPO for input Q1-Q8)**

**- x1 set of 8-bit shift registers (PISO as output Q9-Q16(labeled P))**


(b) For each bit slice, show the gate-level design and layout design. For layout, include the snapshot from Cadence Virtuoso. If you have used any other blocks, include them as well.

Full Adder:

*Full Adder (Textbook Reference): ✓*

 

 
*Full Adder in Cadence Virtuoso (Layout XL): ✓*



Full Adder Truth Table: ✓


Inputs			Outputs	
A	B	C – IN	Sum	C – Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 Full Adder Waveform in Calibre (ADE L): ✓




Full Adder with AND gate:

 *AND in Virtuoso (Layout XL, using NAND + Inverter): ✓*




*AND Waveform in Calibre (ADE L): ✓*

 


*Full Adder w/ AND gate: ✓*

**A = high, B = high**

 


*Full Adder w/ AND continued... ✓*

$A = \text{high}, B = \text{low}$

 

Full Adder w/ AND layout ✓

 





Registers (**Input** and **Output**):

**Inputs:** ✓

Shift registers SIPO X

 


Shift registers SIPO Y

 


**Outputs:** ✓


The first 4 (Far right PISO Outputs)

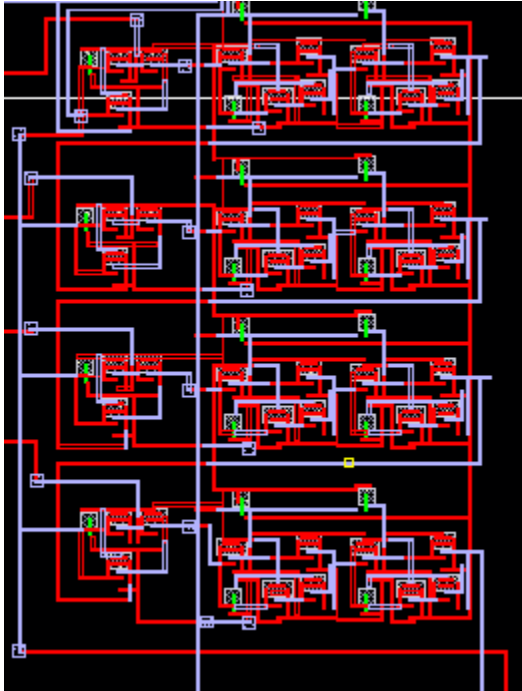

The second 4

 

4x4 array multiplier: ✓

 

Reference:


 


Figure 2: Bit-sliced array multiplier example

Multiplier (4x4 array) waveform: ✓

Vector tested: 1111 \* 1111

 


Ring Oscillator (If used):

Not applicable

(10 pts.) Show the layout of your multiplier with the registers.

Final Product: ✓

 

*note: bounding box area fits within the 900x900 constraint*

**(10 pts.)** Explain the design and functionality of your multiplier.


Our 4x4 bit-sliced array multiplier shown in the images of this pdf report were our hardware layout implementation of binary multiplication. It takes two 4-bit binary numbers, X ( $x_3x_2x_1x_0$ ) and Y ( $y_3y_2y_1y_0$ ), as inputs and produces an 8-bit product as the output, using SIPO input registers and PISO output registers. The design creates partial products for each bit of X multiplied by each bit of Y. These partial products are then summed using Carry Save Adder.

The inputs are taken in serially from X and Y pins in the design. In the input of Y, there is a MUX that determines whether the design is in test mode or normal mode. If in normal mode, the X and Y take a serial in input, make it into a parallel output, and input those values into the multiplier. The result of the multiplication is the input into a parallel in serial out shift register, where the parallel inputs is the 8-bit results, and the output is the 8 serial bits. Before each shift register, there is a also a MUX that uses the same TEST signal to determine whether the output registers should take the inputs from the multiplier, or input from the input registers X and Y. Once in test mode, the X register takes a serial input, the last register in X is connected the first in Y, and the last in Y is connected to the first of the output register. This makes a large 16-bit shift register that is tested to ensure the full functionality of all of the registers.


**(20pts) Simulation Results:**

(10 pts total) Individual cells:

Full Adder: ✓

 


Full Adder with AND gate: ✓

 


Registers (Test Mode):

11111111 ✓

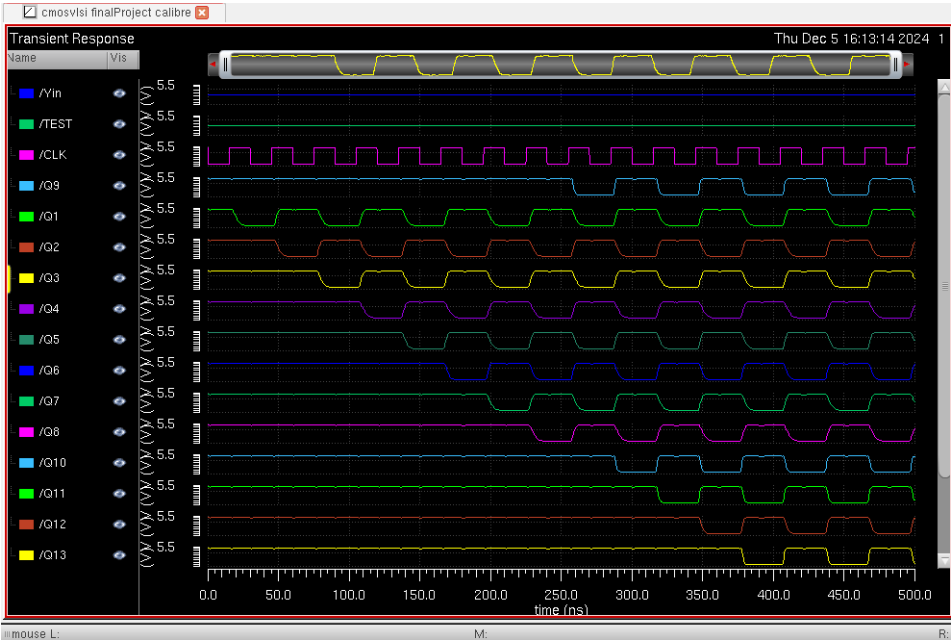

00000000 ✓

 

Ring Oscillator (If used):

N/A




(10 pts) The final multiplier in test and normal modes:

## **8 Test vectors (Normal modes)**


*Note: Outputs are read from Q16 (labeled P) to Q9.*

*Q8 was an input bit that was left on when plotting waveforms and can be disregarded in the following screenshots.*

 
### **Test vector 1) $1001 * 1001 = 0101\ 0001$**



 
## Test vector 2) $1111 * 0011 = 0010\ 1101$



 
## Test vector 3) $1001 * 1011 = 0111\ 0101$



 
**Test vector 4)  $0011 * 0011 = 0000\ 1001$**



 
**Test vector 5)  $1111 \times 1111 = 1110\ 0001$**



 
**Test vector 6)  $0000 * 0000 = 0000\ 0000$**



 
**Test vector 7) 1111\*0000 = 0000 0000**



 Test vector 8)  $1001 * 0011 = 0001\ 1011$



Test Mode (TEST=High) ✓

 

above image (TEST=1) shows parallel shift through registers, creating the honeycomb-like waveform output.